



CSE 201: DIGITAL LOGIC DESIGN

ENCODER, PRIORITY ENCODER, MULTIPLEXER

Prepared By

Lec Sumaiya Afroz Mila

CSE, MIST

ENCODER

- Does reverse operation to decoder
- An encoder has 2^n **(or fewer)** input lines and n output lines
- Constraint – only one input is active at a time
- An **encoder** is a digital circuit that has **2^n or fewer input lines** and **n output lines**.
The output lines generate the binary code corresponding to the input value
- Example – Octal to binary encoder
 - Has 8 inputs, one for each octal digit
 - 3 outputs, that generates the corresponding binary number
 - It is assumed that, **only one input has a value of 1 at a given time**



ENCODER

D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	X	Y	Z
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Octal to Binary encoder truth table

$$X = D_7 + D_6 + D_5 + D_4$$

$$Y = D_7 + D_6 + D_3 + D_2$$

$$Z = D_7 + D_5 + D_3 + D_1$$


 


FIGURE 5-13
Octal-to-binary encoder

ENCODER

- Limitations of the previous encoder –
 - **Only one input can be active at any given time:** If two inputs are active simultaneously, output produces undefined combination. I.e. If D_3 and D_6 are active at the same time, output of the encoder will be 111 which is neither binary 3 nor binary 6. **To solve this limitation, priority encoder is introduced.**
 - When all the inputs are 0, output of the encoder will be 000. Again, output of the encoder will be 000 if D_0 is equal to 1. This can be resolved by providing an additional output indicating that none of the inputs are active.

 

PRIORITY ENCODER

- A priority encoder is a special type of encoder circuit that includes priority function
- Multiple inputs maybe active at the same time
- Highest priority input gets the precedence
- D_3 has the highest priority, then D_2 has the second highest priority and so on.

Truth Table of a Priority Encoder


Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

- When input D_3 is equal to 1, **regardless of the values of the other inputs**, output for XY will be 11(binary 3)
- As D_2 has the second highest priority level, when $D_2 = 1$, regardless of the values of the other two lower priority inputs(D_1 and D_0), the output for XY will be 10, given that **D_3 must be equal to 0**
- A **Valid-output** indicator, set to 1 when one or more of the inputs are active
- When all inputs are inactive, $V=0$, other two outputs of the circuit are not used

PRIORITY ENCODER

Truth Table of a Priority Encoder

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

 

$$x = D_2 + D_3$$

$$y = D_3 + D_1 D'_2$$

$$V = D_0 + D_1 + D_2 + D_3$$

$D_0 D_1$		$D_2 D_3$			
		00	01	11	10
D_0	00	m_0 X	m_1 1	m_3 1	m_2 1
	01	m_4	m_5 1	m_7 1	m_6 1
	11	m_{12}	m_{13} 1	m_{15} 1	m_{14} 1
	10	m_8	m_9 1	m_{11} 1	m_{10} X

$x = D_2 + D_3$

$D_0 D_1$		$D_2 D_3$			
		00	01	11	10
D_0	00	m_0 X	m_1 1	m_3 1	m_2
	01	m_4 1	m_5 1	m_7 1	m_6
	11	m_{12} 1	m_{13} 1	m_{15} 1	m_{14}
	10	m_8	m_9 1	m_{11} 1	m_{10}


$y = D_3 + D_1 D'_2$

PRIORITY ENCODER

$$x = D_2 + D_3$$


$$y = D_3 + D_1 D_2'$$

$$V = D_0 + D_1 + D_2 + D_3$$

 

MULTIPLEXER

- A **digital multiplexer** is a combinational circuit that selects binary information from **one of many input lines** and directs it to a **single output line**
- There are **n selection lines** whose bit combinations determine which input is selected.
- Generally there are 2^n input lines, n selection lines
- Each of the two input lines **I_0 and I_1** applied to one input of an AND gate
- Selection line **S** decoded to select a particular AND gate

 


2 to 1 line multiplexer

4 TO 1 LINE MULTIPLEXER

- In this circuit, there are **4 input lines, 2 selection lines**
- Each of the four input lines I_0 to I_3 applied to one input of an AND gate
- Selection lines S_1 and S_0 decoded to select a particular AND gate


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 Function table of a 4 to 1 line multiplexer



 (c) Block diagram

Block diagram of a 4 to 1 line multiplexer




4 to 1 line multiplexer

4 TO 1 LINE MULTIPLEXER

- When $S_1S_0=10$, AND gate associated with I_2 has **two of its input equal to 1** and the **third input is connected to I_2** .
- Other 3 AND gates has atleast one input equal to 0, making their output equal to 0
- The OR gate output is now equal to the value of I_2


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 Function table of a 4 to 1 line multiplexer



 (c) Block diagram

Block diagram of a 4 to 1 line multiplexer



4 to 1 line multiplexer

FUNCTION IMPLEMENTATION USING MUX

- Any boolean function can be implemented by using a multiplexer
- A boolean function of $n+1$ variables can be implemented by taking n variables to the ***selection lines*** of the multiplexer.
- The remaining variable is used as the input line for the multiplexer

Example- $F(A, B, C) = \sum(1, 3, 5, 6)$

Steps:

1. Choose the selector variables.

Lets choose,

- B, C as selector S_1 and S_0
- A as input line



FUNCTION IMPLEMENTATION USING MUX

Example- $F(A, B, C) = \sum(1, 3, 5, 6)$

Steps:


2. In the first row, list the name of the input lines of the multiplexers horizontally
3. In the second row, list the minterms where A is complemented
4. In the third row, list the minterms where A is uncomplemented
5. Circle the minterms for which the function outputs 1
6. Fourth row presents the multiplexer inputs
 - If the two minterms in a column are not circled, apply 0 to the corresponding multiplexer input
 - If the two minterms in a column are circled, apply 1 to the corresponding multiplexer input
 - If the bottom minterm is circled and the top is not circled, apply A to the corresponding multiplexer input
 - If the top minterm is circled and the bottom is not circled, apply A' to the corresponding multiplexer input



FUNCTION IMPLEMENTATION USING MUX

$$F(A, B, C) = \sum(1, 3, 5, 6)$$


MUX input line	I ₀	I ₁	I ₂	I ₃
A'	0	1	2	3
A	4	5	6	7
Input values	0	1	A	A'

 

FUNCTION IMPLEMENTATION USING MUX

$$F(A, B, C) = \sum(1, 2, 4, 5)$$

MUX input line	I_0	I_1	I_2	I_3
A'	0	1	2	3
A	4	5	6	7
Input values	A	1	A'	0

 


FUNCTION IMPLEMENTATION USING MUX

- It is not necessary to choose the leftmost variable in the ordered sequence of a variable list for the data inputs of the multiplexer. Any of the variable can be chosen to be the input
- $F(A, B, C) = \sum(1, 2, 4, 5)$

MUX input line	I_0	I_1	I_2	I_3
Z'	0	2	4	6
Z	1	3	5	7
Input values	Z	Z'	1	0

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

SELF STUDY

- Why is a multiplexer called data selector?
- Logic diagram of a *quadruple 2 to 1 line multiplexer*.
- Implement the following function with a multiplexer

$$F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$$

