



CSE 201: DIGITAL LOGIC DESIGN

SR LATCH, MEMORY ELEMENTS

Prepared By

Lec Sumaiya Afroz Mila

CSE, MIST

SEQUENTIAL CIRCUIT

- ❑ Consist of a **combinational circuit** to which **storage elements** are connected to form a feedback path
- ❑ The storage elements are devices capable of storing binary information.
- ❑ **State of a circuit:** Binary information stored in these elements at any given time
- ❑ The state of the memory devices now, also called current state
- ❑ **Next states and outputs** are functions of **inputs and present states of storage elements**
- ❑ Memory elements examples- latch, flip-flop

 



Fig. 5-1 Block Diagram of Sequential Circuit

LATCH

- ❑ Can store binary information(0 or 1) indefinitely (as long as power is provided)
- ❑ Building block or basic circuit of other memory elements
- ❑ Level-triggered memory element
- ❑ Constructed with NOR gates or NAND gates



SR LATCH

 

(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	Forbidden	

Memory


Memory

Truth Table of NOR gate

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0



SR LATCH

 

S	R	Q	Q'
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	Forbidden	

Memory

Memory

Truth Table of NAND gate

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0



TWO TYPES OF SEQUENTIAL CIRCUIT

□ Asynchronous sequential circuit


- Depends upon the input signals at any instant of time and their change order
- Hard to design
- Works faster as there is no clock
- Status of the memory element is affected any time as soon as the input is changed
- Example - Latch

□ Synchronous sequential circuit


- Defined from the knowledge of its signals at discrete instants of time
- Much easier to design
- Works slower
- Status of the memory element is affected only at the active edge of clock if input is changed
- Example – flip flop



SYNCHRONOUS CLOCKED SEQUENTIAL CIRCUIT

 

(a) Block diagram

 

(b) Timing diagram of clock pulses

Fig. 5-2 Synchronous Clocked Sequential Circuit



MEMORY ELEMENTS

- Latch — a **level-sensitive** memory element

Examples -

- SR latches
- D latches

- Flip-Flop — an **edge-triggered** memory element



Positive Edge



Negative Edge

Examples-

- Master-slave flip-flop
- Edge-triggered flip-flop

- RAM and ROM — a mass memory element

