

So, if we add one more diode in series with D1 & D2, P point need more voltage to drive rest active elements.

4.6 calculate the value of h_{FE} required for a fan-out of 10 in the DTL gate at fig 4.12

For all inputs are high

Applying KCL at the base of Transistor T₁

$$I_L \times N + I_C = I_{C(max)}$$

$$h_{FE} = \frac{I_C}{I_B}$$

$$I_1 = I_2 + I_B$$

$$I_B = I_1 - I_2 \quad \text{--- (1)}$$

$$V_P = 0.7 + 0.7 + 0.8 = 2.2 \text{ V}$$

$$I_1 = \frac{V_{CC} - V_P}{R} = \frac{(5 - 2.2) \text{ V}}{5 \text{ k}\Omega} = 0.56 \text{ mA}$$

$$I_2 = \frac{V_{BE(sat)}}{R_B} = \frac{0.8 \text{ V}}{5 \text{ k}\Omega} = 0.16 \text{ mA}$$

From equation (1)

$$I_B = I_1 - I_2 = (0.56 - 0.16) \\ = 0.4 \text{ mA}$$

The collector currents (without load gates connected) is

$$I_C = \frac{V_{CC} - V_{CE(sat)}}{R_C} \\ = \frac{(5 - 0.2) \text{ V}}{2.2 \text{ k}\Omega} = 2.182 \text{ mA}$$

Now,

~~we know,~~
$$I_L = \frac{V_{CC} - V_P}{R_L}$$

~~$I_L =$~~

Now, ON Load part
From V_{cc} , all current will flow
to DA,

$$\text{At this point, } V_P = (0.7 + 0.2) V \\ = 0.9 V$$

$$I_L = \frac{V_{cc} - V_P}{R} \\ = \frac{(5 - 0.9) V}{5 K\Omega} = 0.82 \text{ mA}$$

Now,

$$I_{c(\max)} = I_L \times N + I_c \\ = 0.82 \times 10 + 2.18 \\ = 10.38 \text{ mA}$$

Now,

$$h_{fe} = \frac{\cancel{I_B}}{\cancel{I_c}} = \frac{I_c}{I_B} \\ = \frac{10.38}{0.4} = 25.95$$

4.5

pg: 122 pg

Fig on: 92 pg

a) what will happen in the DTL circuit ^{if} none of the diodes D1 or D2 is removed?

Answer: when D1 & D2 exist in circuit the required voltage in P point to drive D1, D2 & transistor is

$$V_P = (0.6 + 0.7 + 0.8) = \cancel{2.2V} / 1.7V$$

~~when~~
For all input high

When D1 & D2 both present in circuit

Miss class & ক্যানো Math(a) এর
Case 1 ~~পূর্ণাঙ্গ~~ করে fan out এর করে দেখাবে.

+

For all input high

if D1 or D2 removed.

So, assuming diode D1 to be conducting
& Transistor T to be in saturation,
the voltage $V_P = 0.7 + 0.8 = 1.5V$

Applying KCL at base of T,

$$I_1 = I_B + I_2$$

$$I_B = I_1 - I_2$$

$$I_1 = \frac{V_{CC} - V_P}{R}$$

$$= \frac{(5 - 1.5)V}{5k\Omega}$$

$$I_1 = 0.7mA$$

$$\text{and, } I_2 = \frac{V_{BE(sat)}}{R_B} = \frac{0.8}{5\Omega} = 0.16mA$$

$$I_B = 0.7 - 0.16 = 0.54mA$$

The collector current (without load gate connected) is $I_C = \frac{V_{CC} - V_{CE(sat)}}{R_C}$

$$= \frac{5 - 0.2}{2.2} = 2.182 \text{ mA}$$

Again,

$$h_{FE} = \frac{I_C}{I_B}$$

~~h_{FE}~~

$$I_C = h_{FE} \cdot I_B$$

$$= 30 \times 0.54$$

$$= 16.2 \text{ mA}$$

[consider $h_{FE} = 30$]

$$I_C (2.182 \text{ mA})$$

Load Side

$$V_P = (0.7 + 0.2) = 0.9$$

$$I_L = \frac{V_{CC} - V_P}{R} = \frac{5 - 0.9}{5} = 0.82 \text{ mA}$$

Now,

$$I_L \times N + I_C \leq I_C(\text{Max})$$

$$0.82 \times N + \frac{16.2}{2.182} \leq 16.2$$

$$0.82N \leq 14.018$$

$$N \leq 17.09$$

$$N \approx 17$$

Previously when 2 diode were present

$$N \approx 12$$

So after removing one diode
the amount of fanout increases.

b) What will happen in the DTL circuit if one more diode D_3 is inserted in series with D_1 and D_2

Ans: For all input 1
when D_1 & D_2 both are present
+ Miss V_{CE} class V_{CE} not match
(a) V_{CE} part for case 1

For all input 1
when D_3 is inserted in series with
 D_1 & D_2
so ~~am~~ assuming diode D_1, D_2, D_3
to be conducting and transistor T to
be in saturation, the voltage
 $V_P = (0.7 + 0.7 + 0.7 + 0.8) = 2.9V$

Applying KCL at the base of T_1

$$I_1 = I_B + I_2$$

$$I_B = I_1 - I_2$$

$$I_1 = \frac{V_{CC} - V_P}{R} = \frac{5 - 2.9}{5} = 0.42 \text{ mA}$$

$$I_2 = \frac{V_{BE(sat)}}{R_B} = \frac{0.8}{5 \text{ K}\Omega} = 0.16 \text{ mA}$$

$$I_B = (0.42 - 0.16) \text{ mA} = 0.26 \text{ mA}$$

$$\cancel{I_E} = \frac{I_C}{I_B}$$

$$\cancel{I_E} = \cancel{h_{FE}} I_B =$$

The collector current (without load
gates connected

is
$$I_C = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$

$$= \frac{5 - 0.2}{2.2 \text{ K}\Omega} = 2.182 \text{ mA}$$

Again,

$$h_{FE} = \frac{I_C}{I_B}$$

$$I_C = h_{FE} \times I_B$$

$$= 30 \times 0.26 = 7.8 \text{ mA} \quad \left\{ \begin{array}{l} I_C \\ (2.182) \end{array} \right.$$

For Load Part

$$I_L = \frac{V_{CC} - V_P}{R}$$

$$= \frac{5 - 0.9}{5} = 0.82 \text{ mA}$$

Now,

$$I_L \times N + I_C \leq I_C$$

$$0.82 \times N + 2.182 \leq 7.8$$

$$N \leq 6.85 \approx 6$$

Previously when there is 2 diode

$$N \approx 12$$

Now after adding one more we
get less