



# **CSE 201: DIGITAL LOGIC DESIGN**

## **BCD ADDER, MAGNITUDE COMPARATOR, DECODER, DEMULTIPLEXER**

**Prepared By**


**Lec Sumaiya Afroz Mila**

**CSE, MIST**

# BINARY CODED DECIMAL

- Binary coded decimal (BCD) is a system of writing numerals that assigns a four-digit binary code to each digit 0 through 9 in a decimal (base-10) numeral.
- Numbers **larger** than 9, having two or more digits in the decimal system, are expressed digit by digit. For example, the BCD rendition of the number 1895, (base-10) is

0001 1000 1001 0101

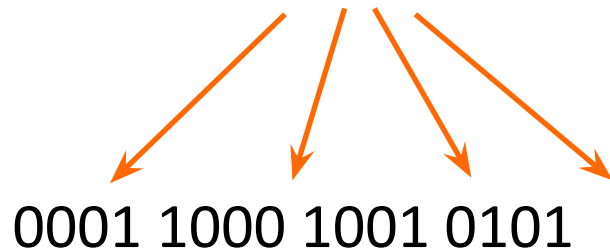

Decimal	BCD	Binary
0	0000	0000
1	0001	0001
2	0010	0010
3	0011	0011
4	0100	0100
5	0101	0101
6	0110	0110
7	0111	0111
8	1000	1000
9	1001	1001



# BCD ADDER

- We will perform addition operation of two decimal numbers in BCD
- Each input does not exit 9
- Sum output will be highest: 19

$$\begin{array}{r} 9(\text{augend}) \\ +9(\text{addend}) \\ +1(\text{input carry}) \\ \hline 19 \end{array}$$

- The binary value and BCD value of the augend and addend are same
- Apply the BCD value of the augend and the addend to a 4-bit binary adder
- Adder will form the sum in binary and produce a result that may range from 0 to 19
- This binary result should be converted to BCD



# BCD ADDER

K	Binary Sum				BCD Sum				
	Z <sub>8</sub>	Z <sub>4</sub>	Z <sub>2</sub>	Z <sub>1</sub>	C	S <sub>8</sub>	S <sub>4</sub>	S <sub>2</sub>	S <sub>1</sub>
0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	0	0	1	0
0	0	0	1	1	0	0	0	1	1
0	0	1	0	0	0	0	1	0	0
0	0	1	0	1	0	0	1	0	1
0	0	1	1	0	0	0	1	1	0
0	0	1	1	1	0	0	1	1	1
0	1	0	0	0	0	1	0	0	0
0	1	0	0	1	0	1	0	0	1
1	1	0	1	0	1	0	0	0	0
1	1	0	1	1	1	0	0	1	0
1	1	1	0	0	1	0	0	1	1
1	1	1	0	1	1	0	1	0	0
1	1	1	1	0	1	0	1	0	1
1	1	1	1	1	1	0	1	1	0
1	0	0	0	0	1	0	1	1	0
1	0	0	0	1	1	0	1	1	1
1	0	0	1	0	1	1	0	0	0
1	0	0	1	1	1	1	0	0	1

8



# BCD ADDER

- From the table, when binary sum  $\leq 1001(9_{10})$ , corresponding BCD is identical – **No conversion needed**
- When binary sum  $> 1001$ , it becomes non-valid as BCD – **conversion needed**
  - For binary sum  $> 1001$ , we have to convert it to a valid BCD representation
  - When binary sum is 1010, decimal is 10 – correct BCD representation will be

0001 0000



- To convert 1010 to 10000, we have to add  $(0110)_2$  or  $(6)_{10}$  with 1010
- Similarly if we add  $(0110)_2$  or  $(6)_{10}$  with 1011.....10011, we will get the corresponding BCD representation



# BCD ADDER

- Now we have to design the circuit.
- We have to design a circuit that will detect when conversion should be performed and when not.

From the table, it is visible that, **conversion is needed** when the binary sum has an output carry **K=1**.

Other 6 combinations  
From 1010 to 1111 that  
Need conversion have a 1 in position  $z_8$

- To distinguish them from the value 1000 and 1001 (also have a 1 in position  $z_8$ ), we specify, either  $z_4$  or  $z_2$  must have a 1


$$C = K + Z_8 Z_4 + Z_8 Z_2$$

K	$z_8$	$z_4$	$z_2$	$z_1$	C	$s_8$	$s_4$	$s_2$	$s_1$			
0	1		0	0	0		0	1	0	0	0	0
0	1		0	0	1		0	1	0	0	0	1
0	1		0	1	0		1	0	0	0	0	0
0	1		0	1	1		1	0	0	0	1	1
0	1		1	1	0		1	0	1	0	0	0
0	1		1	1	1		1	0	1	1	0	1
1	0		0	0	0		1	0	1	1	1	0
1	0		0	0	1		1	0	1	1	1	1
1	0		0	1	0		1	1	0	0	0	0
1	0		0	1	1		1	1	0	0	0	1



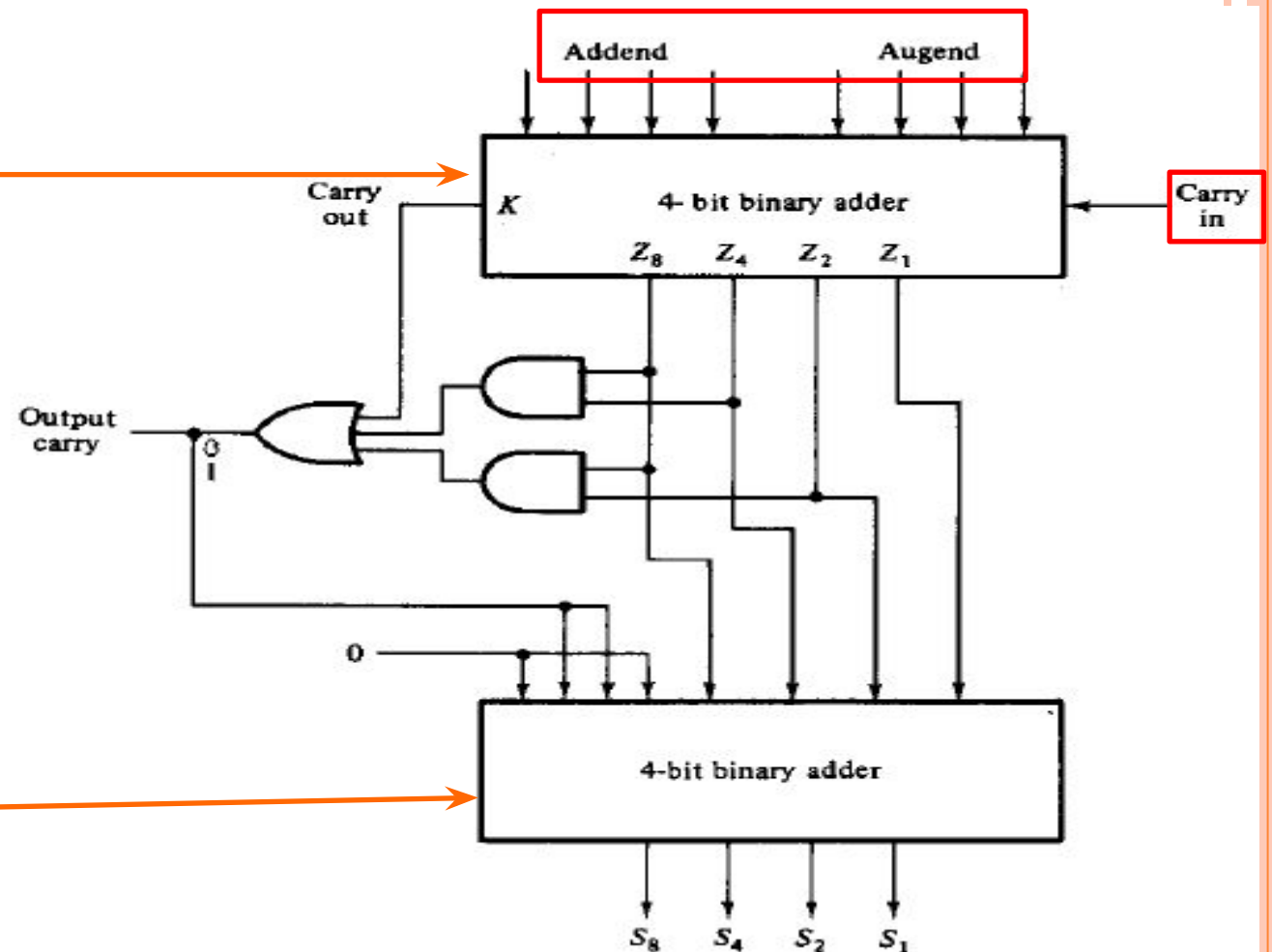
# BCD ADDER

- When  $C = K + Z_8Z_4 + Z_8Z_2$ , it is necessary to add 110 to the binary sum and provide an output carry for the next stage
- To add 0110 to the binary sum, we use a second 4-bit binary adder
- First the **augend, added** and the **input carry** are added in the top 4-bit binary adder to produce the binary sum
- When output **carry=0 nothing added**
- When output **carry=1, binary 0110 is added** to the binary sum through the bottom 4-bit binary adder


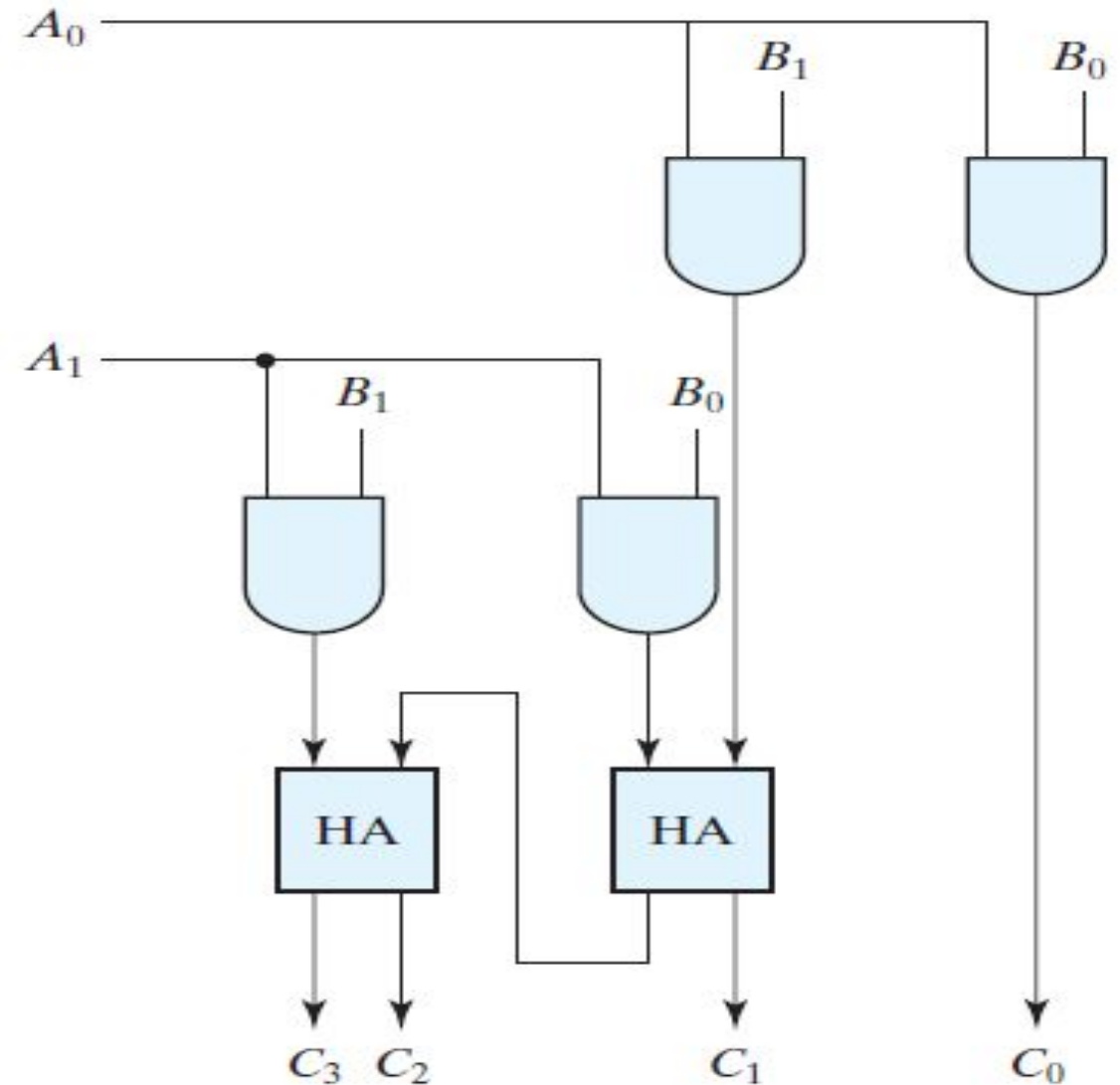
## 2- BIT by 2-BIT BINARY MULTIPLIER

$$\begin{array}{r} \phantom{A_1} B_1 \phantom{00} B_0 \\ A_1 \phantom{00} A_0 \\ \hline A_0 B_1 \phantom{00} A_0 B_0 \\ A_1 B_1 \phantom{00} A_1 B_0 \\ \hline C_3 \phantom{00} C_2 \phantom{00} C_1 \phantom{00} C_0 \end{array}$$





# MAGNITUDE COMPARATOR

- **Magnitude Comparator:** A *magnitude comparator* is a combinational circuit that compares two numbers A and B, and determines their relative magnitudes. The **outcome** of the comparison is specified by **three binary variables** that indicate whether  $A=B$ ,  $A>B$ , or  $A<B$
- The circuit for comparing two n-bit numbers has  $2^{2n}$  entries in the truth table and becomes too cumbersome even with  $n=3$ .
- So, we will develop an algorithm to design a comparator



# MAGNITUDE COMPARATOR

- We will consider two 4-bit numbers:

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

- The two numbers are **equal** if **all pairs** of significant **digits are equal**. If  $A_3=B_3$  &  $A_2=B_2$  &  $A_1=B_1$  &  $A_0=B_0$

- So the equality relation of each pair of bits will be

$$x_i = A_i B_i + A_i' B_i' , \text{ where } x_i=1 \text{ only if the pair of bits in position } i \text{ are equal}$$

- If all pair of bits of A and B are equal which means, if  $X_3 X_2 X_1 X_0$  all are equal 1, we can say  $A=B$



# MAGNITUDE COMPARATOR

- To determine if  $A > B$  or  $A < B$ , we inspect relative magnitudes of significant bits starting from the MSB
- If these two bits are equal, we compare the next lower significant pair of bits
- This comparison continues until a pair of unequal digits is reached
  - If the corresponding digit of  $A=1$  and that of  $B=0$ , we conclude  $A > B$
  - If the corresponding digit of  $A=0$  and that of  $B=1$ , we conclude  $A < B$
- The boolean function for the above sequential comparison will be:

$A_3$	$A_2$	$A_1$	$A_0$
$B_3$	$B_2$	$B_1$	$B_0$

1	1	1	1
1	1	0	1

1	1	0	1
1	1	1	1

$$(A > B) = A_3 B'_3 + x_3 A_2 B'_2 + x_3 x_2 A_1 B'_1 + x_3 x_2 x_1 A_0 B'_0$$

$$(A < B) = A'_3 B_3 + x_3 A'_2 B_2 + x_3 x_2 A'_1 B_1 + x_3 x_2 x_1 A'_0 B_0$$



# MAGNITUDE COMPARATOR

If  $A_3 B_3' = 1$ ,  $A > B$

$A_3$	$A_2$	$A_1$	$A_0$
$B_3$	$B_2$	$B_1$	$B_0$

1	1	1	1
0	1	0	1

If  $X_3 A_2 B_2' = 1$ ,  $A > B$

1	1	0	1
1	0	1	1

If  $X_3 X_2 A_1 B_1' = 1$ ,  $A > B$

1	1	1	1
1	1	0	1


If  $X_3 X_2 X_1 A_0 B_0' = 1$ ,  $A > B$

1	1	1	1
1	1	1	0

$$(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$

$$(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$$

# MAGNITUDE COMPARATOR

 

# MAGNITUDE COMPARATOR

- $x_i = A_i B_i + A_i' + B_i'$
- $(A_0' B_0 + A_0 B_0')' = (A_0 \text{ xor } B_0)'$   
= A0 xnor B0  
=  $A_0 B_0 + A_0' B_0'$




# DECODER

- A *decoder* is a combinational circuit that converts binary information from *n-input* lines to a maximum  *$2^n$  unique output lines*.
- If the *n-bit* decoded information has **unused** or **don't care** combinations, the decoder output will have **fewer than  $2^n$  outputs**
- These decoders are called *n-to-m-line* decoders, where  $m \leq 2^n$
- 1-to-2-Line Decoder -

<b>A</b>	<b>D<sub>0</sub></b>	<b>D<sub>1</sub></b>
0	1	0
1	0	1

(a)

 


(b)



# 2-to-4 Line Decoder

- The 2 inputs are decoded into 4 outputs
- Each output represents one of the minterms of the 2-input variables
- 2 inverters provide the complement of the inputs
- Each one of the 4 AND gates generate one of the minterms

<i>A</i>	<i>B</i>	<i>D</i> <sub>3</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>0</sub>
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 


$$D_3 = AB \quad D_1 = A'B$$

$$D_2 = AB' \quad D_0 = A'B'$$


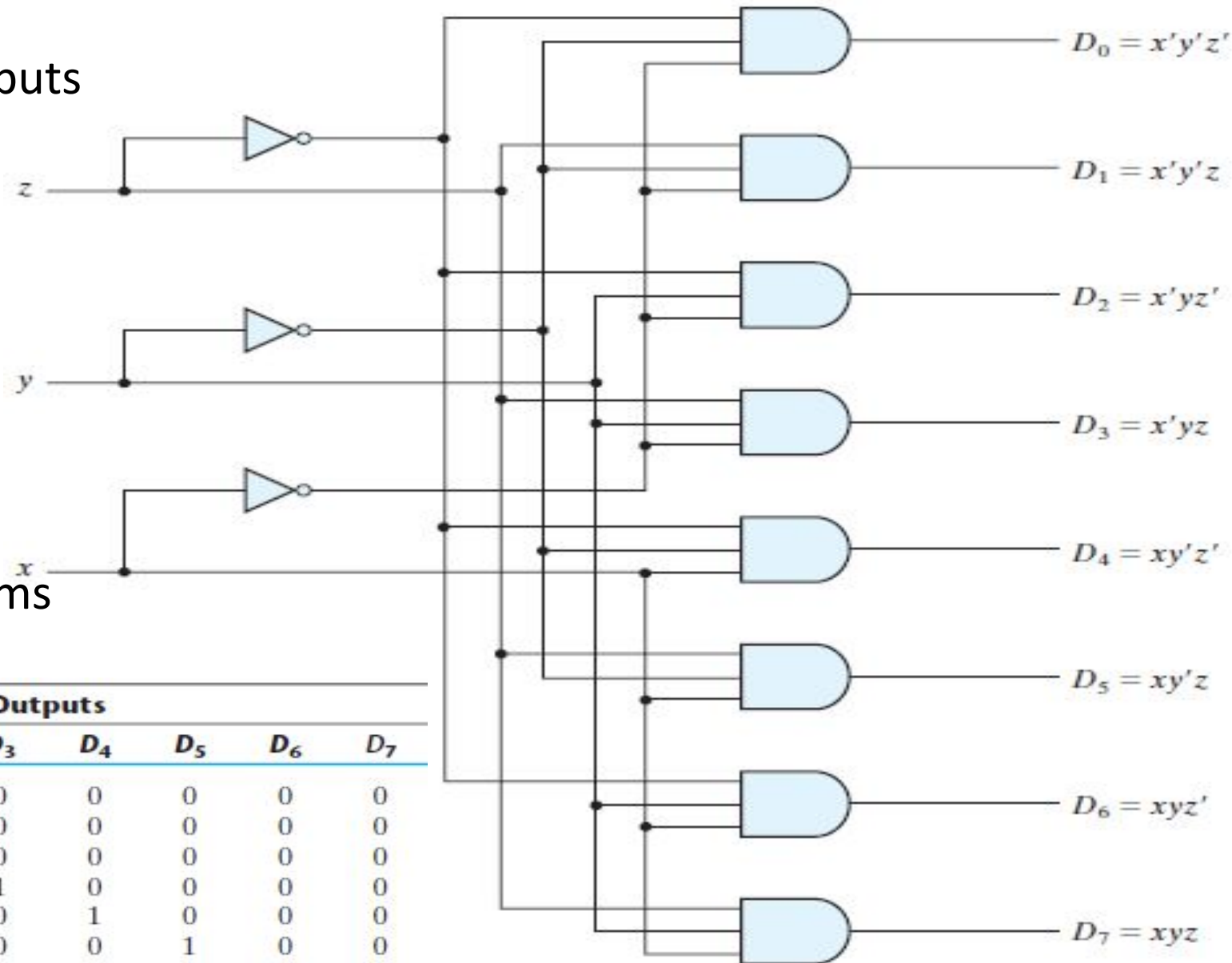
# 3-to-8 Line Decoder

- 3 inputs are decoded into 8 outputs
- Each output represents one of the minterms of the 3-input variables
- 3 inverters provide the complement of the inputs
- Each one of the 8 AND gates generate one of the minterms



Inputs			Outputs							
$x$	$y$	$z$	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

# 3-to-8 Line Decoder

- A particular application of this decoder is binary-to-octal conversion.
- The input variables represent a binary number
- The outputs represent the eight digits of a number in octal number system



## Binary to Octal Conversion




Binary	Octal
0	0
1	1
10	2
11	3
100	4
101	5
110	6
111	7

Inputs			Outputs							
x	y	z	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

# 2-to-4 Line Decoder with enable input



- Some decoders are constructed with **NAND** gates
- May include one or more **Enable** inputs to control the circuit operation
- Circuit operates with **complemented output**
- and **complement enable input**
- The decoder is **enabled** when  $E=0$
- Circuit is disabled when  $E=1$**
- When circuit is disabled, none of the outputs are equal to 0 and none of the minterms are selected
- At any given time, only one output is equal to 0, other outputs are 1

$E$	$A$	$B$	$D_0$	$D_1$	$D_2$	$D_3$
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

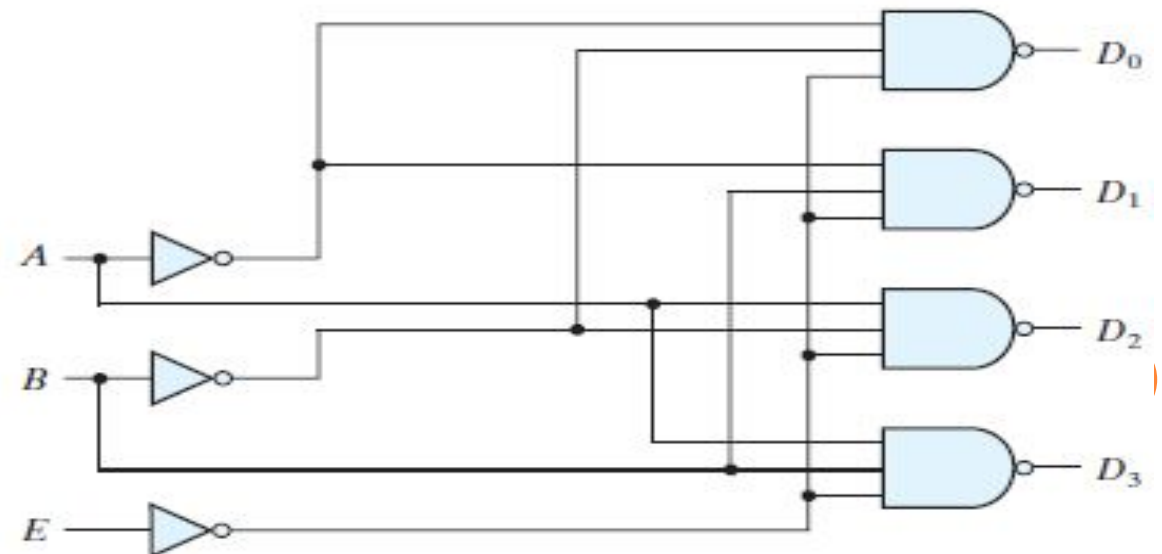
 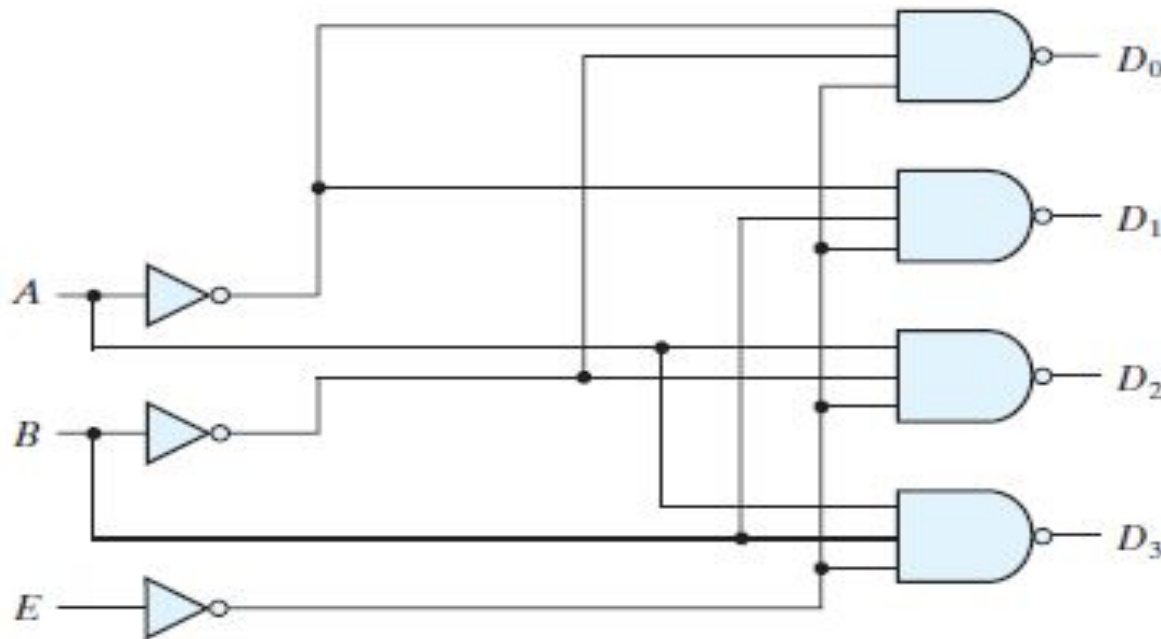
# Decoder

- A decoder can operate with complemented or uncomplemented output
- Enable input may be activated with a 0 or a 1 signal
- Some decoders may have two or more enable inputs
- Block diagram of the 2-to-4 line decoder -



(a) Decoder with enable

# COMBINATIONAL LOGIC IMPLEMENTATION

- A decoder produces  $2^n$  minterms of  $n$ -inputs
- Any boolean function can be expressed in sum of minterms form
- So, a decoder can be used to generate minterms, and an external OR gate to form the sum
- Any combinational circuit can be implemented with a decoder and OR gates
- Implementing a combinational circuit with a decoder and OR gates requires the **boolean function of the circuit be expressed in sum of minterms**



# IMPLEMENTING FULL ADDER USING DECODER

From the table of the full-adder, function for this circuit in sum of minterms:

$$S = X'Y'Z + X'YZ' + XY'Z' + XYZ \quad \text{or} \quad S(x, y, z) = \sum(1, 2, 4, 7)$$

$$C = X'YZ + XY'Z + XYZ' + XYZ \quad \text{or} \quad C(x, y, z) = \sum(3, 5, 6, 7)$$


Full-adder circuit has **3 inputs** and **total 8 outputs**, we need **3-to-8-line decoder**

Decoder generates the 8 minterms for x,y,z

The **OR gate** for **output S** forms the sum of minterms **1,2,4 and 7**


The **OR gate** for **output C** forms the sum of minterms **3,5,6, and 7**

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

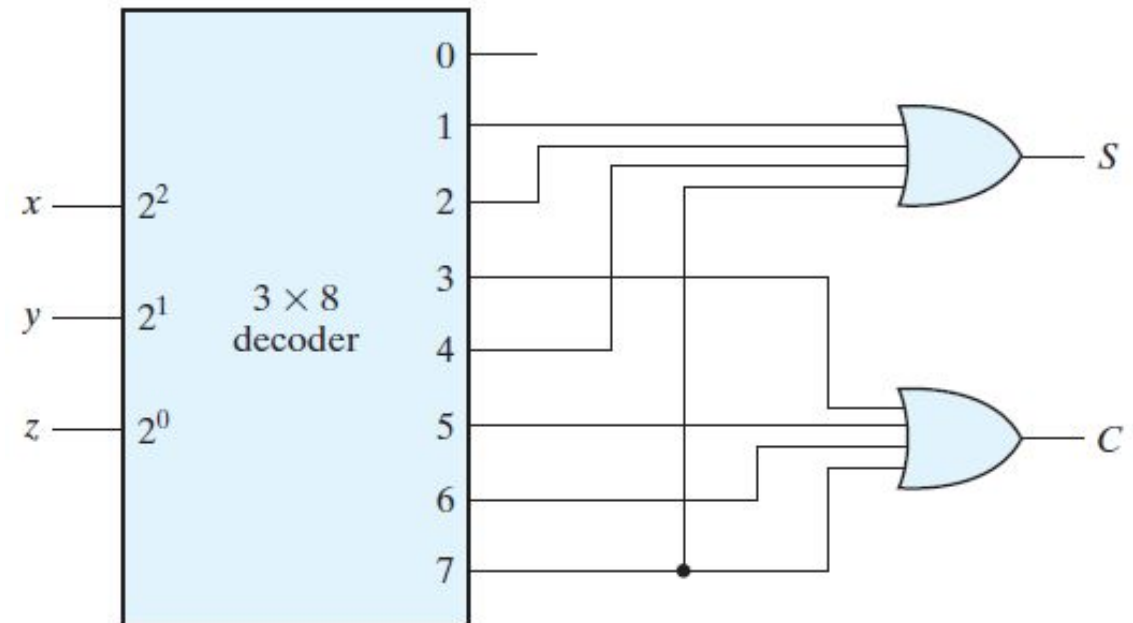

 
# DEMULTIPLEXER

- ❑ **Demultiplexer:** A *demultiplexer* is a circuit that **receives information** from **a single line** and **transmits** this information it to **one of  $2^n$  possible output lines**.
- ❑ The selection of a specific output is controlled by the bit combination of  $n$  selection lines.
- ❑ The decoder can function as **1-to-4-line demultiplexer** when **E** is taken as a **data input line** and **A and B** are taken as the **selection inputs**.




(a) Decoder with enable

 

(b) Demultiplexer
 
# DEMULTIPLEXER

- The single input variable **E** has a path to **all four outputs**, but the input information is **directed** to only **one of the output lines**, as specified by the binary combination of the two selection lines A and B
- Example, if the selection lines **AB = 10**, output **D<sub>2</sub>** will be the **same as the input value E**, while all other outputs are maintained at 1.
- As decoder and demultiplexer operations are obtained from the same circuit, a decoder with an enable input is referred to as a decoder – demultiplexer



(b) Demultiplexer



# DECODER EXPANSION

- Decoder/ Demultiplexer can be connected together to form a larger decoder circuit
- Example, **two 3-to-8-line decoders** with enable inputs connected to form a **4-to-16-line decoder**
- When  $w = 0$ , the *top decoder is enabled* and *the other is disabled*.
- The bottom decoder outputs are all 0's, and the top eight outputs generate minterms 0000 to 0111.
- When  $w = 1$ , the enable conditions are reversed: The *bottom decoder* outputs generate minterms 1000 to 1111, while the *outputs of the top decoder* are all 0's.

